

BLG222E

Computer Organization

Instructors
Gökhan İnce
Mustafa Kamaşak

Project #2
Basic Computer


Rıdvan Sırma- 150120133
Cemal Türkoğlu- 150140719
Çiğdem Duvacı- 150120301
Mehmet Dinçer Bozdoğan-
04008022

We use the Alu Design in project 1

S_3	S_2	S_1	S_0	C (bit 0) in CCR	Operation	Function	Flag updates			
							Z	N	O	C
1	0	0	0	0	$F \leftarrow A$	Transfer A	✓	✓	✓	✓
1	0	0	0	1	$F \leftarrow A + 1$	Increment A	✓	✓	✓	✓
1	0	0	1	0	$F \leftarrow A + B$	Addition	✓	✓	✓	✓
1	0	0	1	1	$F \leftarrow A + B + 1$	Add with carry	✓	✓	✓	✓
1	0	1	0	0	$F \leftarrow A + \bar{B}$	Subtract with borrow	✓	✓	✓	✓
1	0	1	0	1	$F \leftarrow A + \bar{B} + 1$	Subtraction	✓	✓	✓	✓
1	0	1	1	0	$F \leftarrow A - 1$	Decrement A	✓	✓	✓	✓
1	0	1	1	1	$F \leftarrow A$	Transfer A	✓	✓	✓	✓
0	1	0	0	0	$F \leftarrow A \wedge B$	AND	✓	✓	-	-
0	1	0	0	1	$F \leftarrow \overline{A \wedge B}$	NAND	✓	✓	-	-
0	1	1	0	0	$F \leftarrow A \vee B$	OR	✓	✓	-	-
0	1	1	0	1	$F \leftarrow \overline{A \vee B}$	NOR	✓	✓	-	-
0	1	0	1	0	$F \leftarrow A \oplus B$	XOR	✓	✓	-	-
0	1	0	1	1	$F \leftarrow \overline{A \oplus B}$	XNOR	✓	✓	-	-
0	1	1	1	X	$F \leftarrow \bar{A}$	Complement A	✓	✓	-	-
0	0	0	0	0	$F \leftarrow shr A$	Logical shift right A into F	✓	✓	-	-
0	0	0	0	1	$F \leftarrow ashr A$	Arithmetic shift right A into F	✓	✓	-	-
0	0	0	1	0	$F \leftarrow cshr A$	Circular shift right A into F	✓	✓	-	-
0	0	0	1	1	$F \leftarrow shl A$	Logical shift left A into F	✓	✓	-	-
0	0	1	0	0	$F \leftarrow ashl A$	Arithmetic shift left A into F	✓	✓	✓	-
0	0	1	0	1	$F \leftarrow cshl A$	Circular shift left A into F	✓	✓	-	-

Control Inputs (Register)			
LD	INC	CLR	Function
1	1	1	Loads from the input of the register
1	1	0	Loads from the input of the register
1	0	1	Loads from the input of the register
1	0	0	Loads from the input of the register
0	1	1	Increments the contents of the register
0	1	0	Increments the contents of the register
0	0	1	Clears the register
0	0	0	X

OUR 16-BIT Register Design:

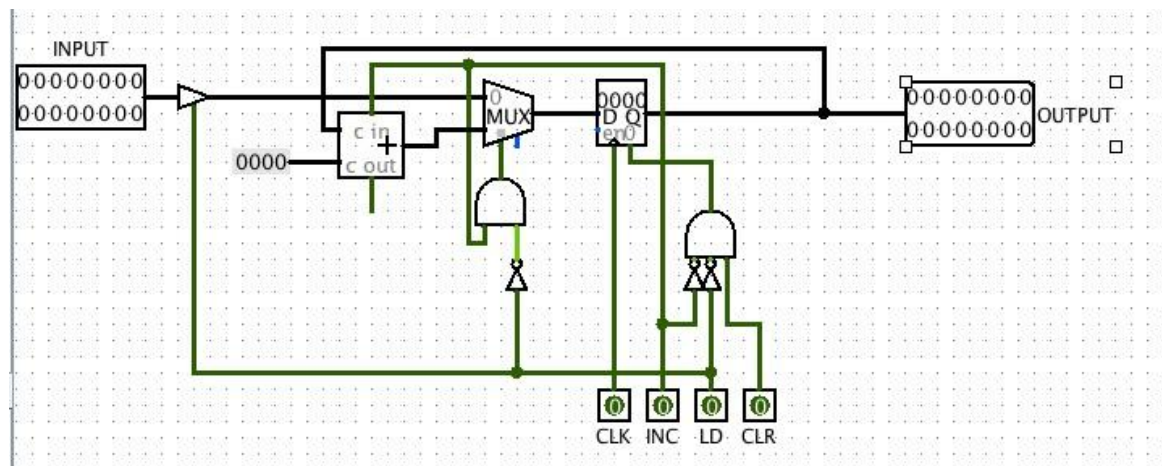

Our Simple Computer

